

DBF Dayanand College of Arts and Science, Solapur

Waveform Generators



Dr. G. S. Shahane
Professor and Head
Department of Electronics
DBF Dayanand College of Arts and
Science, Solapur

ELECTRONICS

Paper VII: Operational Amplifier

Module 2: RC Oscillators

Module Tag: DAYA_ELE_GSS_PVII_C5M1

Table of Contents

- Learning Outcome
- Oscillator
- Conditions for Oscillations
- Phase Shift Oscillator
- Wien Bridge Oscillator

Prerequisites

The student must know

- Types of Waveforms
- Feedback in Amplifier
- Operational Amplifier

Learning Outcome


In this module you will learn about

- Meaning of Oscillator
- Types of Oscillators
- Working of Phase Shift Oscillator
- Working of Wien Bridge Oscillator

Oscillator


- Oscillator is a circuit which generates electrical oscillations of definite wave shape, frequency and amplitude
- Here dc power is used to generate electrical oscillations

Conditions for Oscillations

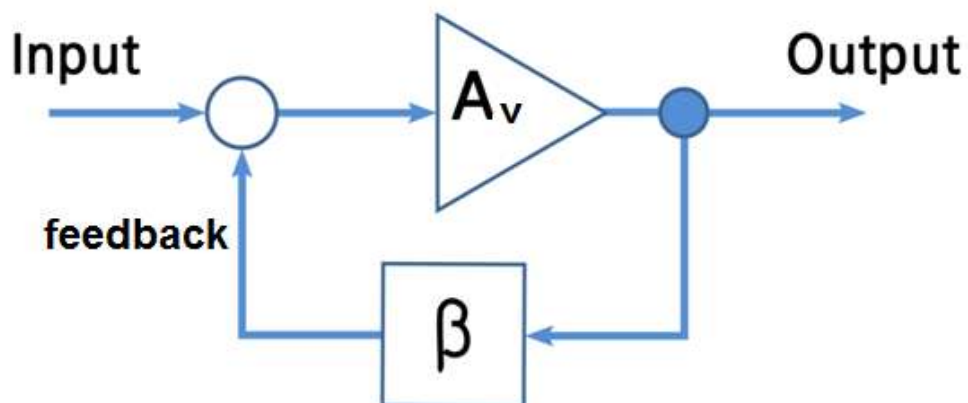


- Barkhausen Criteria
 1. Feedback must be positive
 2. Loop gain (βA_v) must be greater than or equal to one

Types of Oscillators

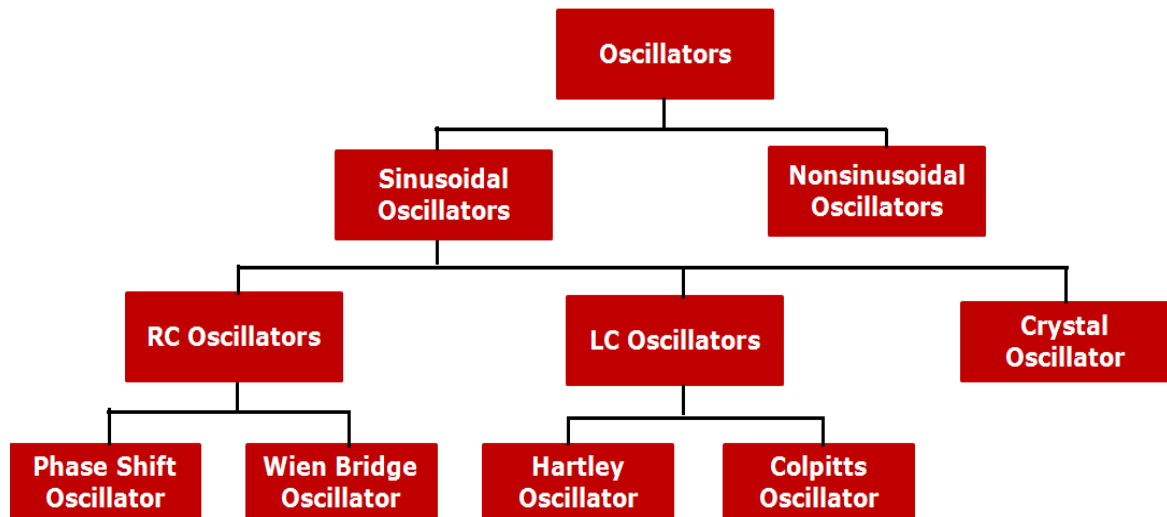

- Depending on the wave shape, oscillators are classified in to two groups
 1. Sinusoidal Oscillator
 2. Nonsinusoidal Oscillator
- Sinusoidal oscillators are classified as
 1. RC Oscillators
 2. LC Oscillators

Op Amp Phase Shift Oscillator

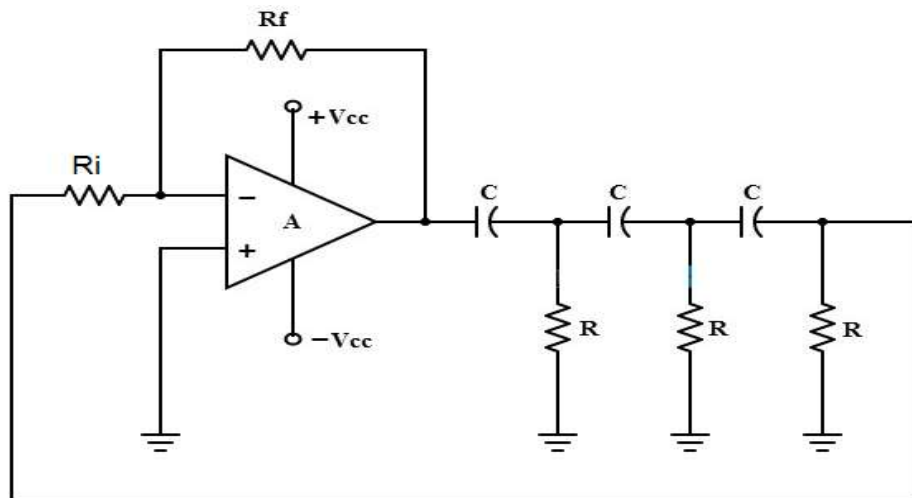

- Op amp works as inverting amplifier and introduces 180° phase shift
- Additional 180° phase shift is introduced by a phase shift network consisting of three RC combinations (each RC network 60° phase shift)
- Thus total phase shift becomes 360° i.e. positive feedback
- Resistors R_i and R_f decides the gain
- Here $\beta=1/29$ Hence for sustained oscillations $A_v \geq 29$
- The frequency of oscillations is given by

$$f = \frac{1}{2\pi\sqrt{6} RC}$$


➤ Advantages

1. It does not require bulky and expensive inductors
2. Since conditions of oscillations are satisfied for only one frequency, the circuit produces pure sine wave
3. Suitable for low frequency oscillations

➤ Disadvantages

1. The circuit is not suitable for variable frequency
2. The circuit is not suitable for high frequency

Wien Bridge Oscillator

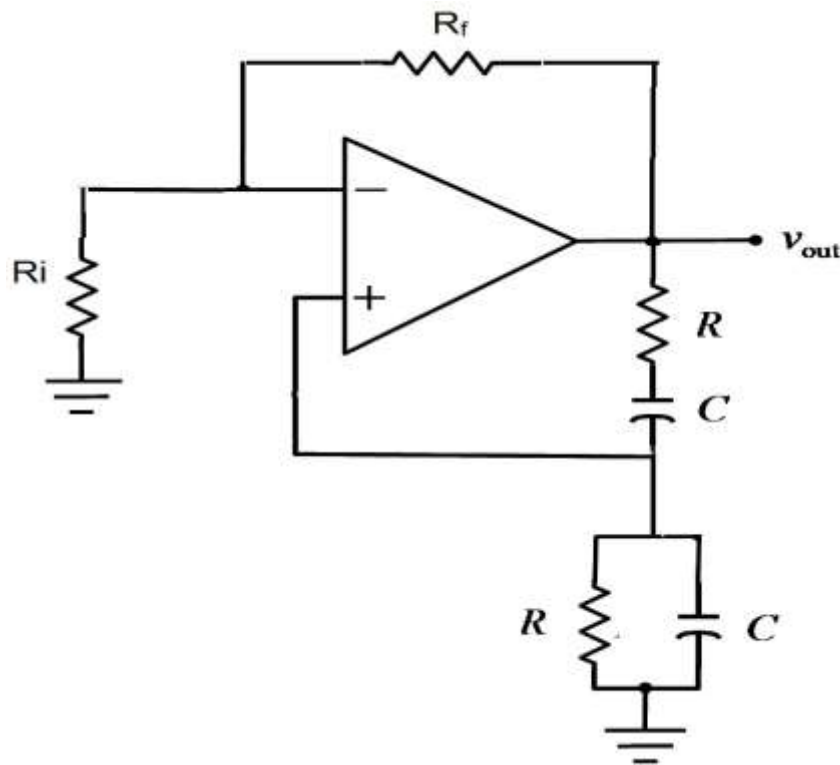

- A Wien Bridge network is used to select the frequency of oscillations.
- It introduces 0° phase shift at a particular frequency
- The feedback factor $\beta=1/3$
- Hence gain of amplifier must be greater than or equal to 3
- The frequency of oscillations is given by

$$f = \frac{1}{2\pi RC}$$

➤ Advantages

1. It does not require bulky and expensive inductors
2. Since conditions of oscillations are satisfied for only one frequency, the circuit produces pure sine wave
3. It gives constant output
4. Suitable for low frequency oscillations
5. The frequency of oscillations can be easily changed

➤ Disadvantages

1. To start oscillations, initially gain must be large
2. It cannot generate high frequency oscillations

Links for Videos and Assignment

Video 1

<https://www.youtube.com/watch?v=Gvb4GIV5iq8>

Video 2

<https://www.youtube.com/watch?v=gbUXbaxvX94>

Source for Videos: All about Electronics from YouTube

Assignment

<https://forms.gle/5DZSw28mYrGPnqNB8>

Additional Resources

1. Linear Integrated Circuit – D. Roy Choudhari, Shail Jain (Wiley Eastern Ltd.)
2. Op-Amps and Linear circuits – Ramakant A. Gaikwad (PHI)
3. Operational Amplifiers and Linear ICs – Caughlin and Driscoll (PHI)
4. Design with Operational Amplifiers and Analog ICs – Franco (McGraw Hill, 2000)